

UNIT TEST - I

B.Sc(CS) First Semester, Examination,2020-21
Subject: Computer System Architecture

Time: 1 Hour]

[Maximum Marks: 30

Note: Question Number 1 is compulsory. Answer any three questions from the remaining.

Q1. (Give answer in short)

Marks : 6X2

- I. Describe X-NOR gate.
- II. Implement AND gate from NOR gate.
- III. Simplify the expression $Y = \overline{(\overline{B} + E)} \cdot (D + \overline{F})$ using De'Morgans Theorem.
- IV. Draw function table and logic circuit of 2 X 1 multiplexer.
- V. Draw function table and logic circuit of 1 X 2 decoder.
- VI. Use two input NAND gate only to implement $Y = (DEFG)'$

SECTION B

Marks:6X3

- Q2) Explain 3X8 decoder in detail.
- Q3) Explain the working of 8 X 1 multiplexer in detail.
- Q4) Describe the working of a binary counter.
- Q5) Describe the working of a SR Flip Flop in detail.
- Q6) a) Solve the following expression by using Boolean laws

$$(A+C)(A+D)(B+C)(B+D)$$

- b) Solve the following expression using K-Map.

$$Y = \sum(0,1,2,3,4,6,8,9,11,13,14,15)$$